

Tutorial 10

Problem 1)

Obtain the expression for the quality factor of a parallel RLC circuit.

Problem 2)


Derive the expressions of the exponential damping coefficient and natural resonant frequency in terms of quality factor.

Problem 3)

- Show that the half-power bandwidth is inversely proportional to the quality factor.
- Show that the resonant frequency is the geometric mean of half-power frequencies.


Problem 4)

A parallel RLC circuit is constructed such that it has the impedance magnitude characteristic plotted in Fig. 15.60. (a) Determine the resistor value. (b) Determine the capacitor value if a 1 H inductor was used. (c) Obtain values for the bandwidth, Q_0 , and both the low half-power frequency and the high half-power frequency.

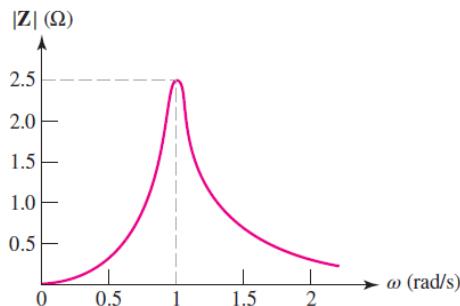

Problem 5)

Find the bandwidth of each of the response curves shown in Figures.

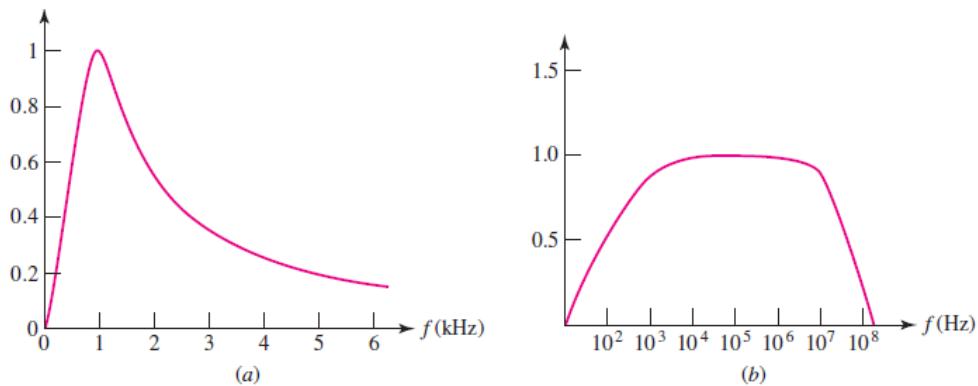

Problem 6)

Design a low-pass filter with a break frequency of 1450 rad/s.

Problem-1

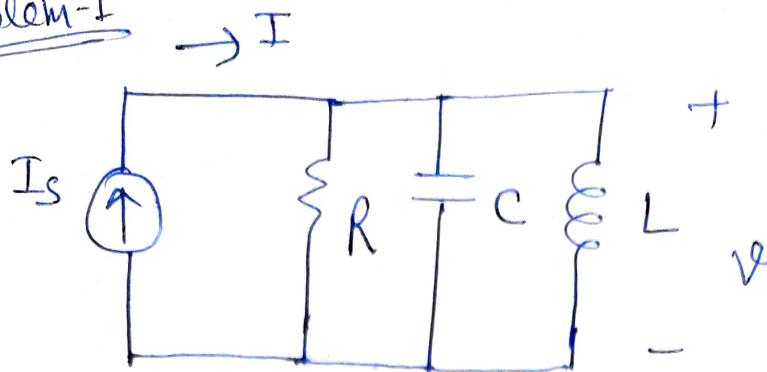


fig: Parallel RLC ckt.

Q = Quality factor:

We define Q as

$$Q = \frac{2\pi \text{ max. energy stored}}{\text{total energy lost per cycle}}$$

$$Q = \frac{2\pi [w_L(t) + w_C(t)]_{\text{max.}}}{P_R T}$$

Q at resonance frequency is denoted by Q_0 .

Now, we select the current forcing function

$$i(t) = I_m \cos \omega_0 t$$

Voltage response at resonance,

$$V(t) = R i(t) = R I_m \cos \omega_0 t$$

The energy stored in capacitor is given by -

~~\otimes~~ $w_C(t) = \frac{1}{2} C V^2$

$$= \frac{I_m^2 R^2 C}{2} \omega_0^2 \sin^2 \omega_0 t$$

The instantaneous energy stored in inductor is given by -

$$\begin{aligned} w_L(t) &= \frac{1}{2} L i_L^2 = \frac{1}{2} L \left(\frac{1}{L} \int v dt \right)^2 \\ &= \frac{1}{2L} \left[\frac{R I_m}{\omega_0} \sin \omega_0 t \right]^2 \\ w_L(t) &= \frac{I_m^2 R^2 C}{2} \sin^2 \omega_0 t \end{aligned}$$

So, The total instantaneous stored energy is therefore constant:

$$w(t) = w_L(t) + w_C(t) = \frac{I_m^2 R^2 C}{2} \text{ (maximum value)}$$

The energy lost in the resistor in one period is the average power absorbed by the resistor

$$\boxed{P_R = \frac{1}{2} I_m^2 R}$$

Now

$$\boxed{P_R T = \frac{1}{2} I_m^2 R}$$

Now By putting all the values in eqⁿ (1)

$$\omega_0 = \frac{2\pi \times I_m^2 R^2 C}{I_m^2 R/2 f_0}$$

$$\boxed{\omega_0 = 2\pi f_0 R C = \omega_0} \quad [2\pi f_0 = \omega_0]$$

Also, by putting $\omega_0 = \frac{1}{\sqrt{LC}}$, we get :

$$\boxed{\omega_0 = R \sqrt{\frac{C}{L}} = \frac{R}{|X_C|} = \frac{R}{|X_L|}}$$

Problem-2

Differential eqⁿ. for parallel RLC Ckt.

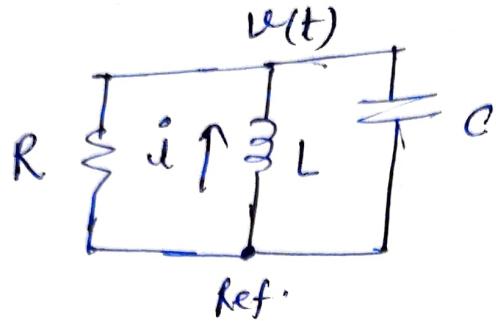


fig: Source free RLC Ckt.

$$\frac{v(t)}{R} + \frac{1}{L} \int v(t) dt + \frac{c}{dt} \frac{dv}{dt} = 0 \quad \textcircled{1}$$

Laplace transform of eqⁿ(1)

$$\frac{V(s)}{R} + \frac{1}{Ls} V(s) + \frac{c}{s} V(s) = 0$$

$$\frac{V(s) \times c}{s} \left[\frac{s}{RC} + \frac{1}{LC} + s^2 \right] = 0$$

$$\frac{V(s) e}{s} \left[s^2 + \frac{1}{RC}s + \frac{1}{LC} \right] = 0$$

$$V(s) \neq 0$$

So

$$s^2 + \frac{1}{RC}s + \frac{1}{LC} = 0$$

$$CS^2 + \frac{1}{R}S + \frac{1}{L} = 0$$

$$S^2 + \frac{1}{RC}S + \frac{1}{LC} = 0$$

$$S_1, S_2 = -\frac{1}{RC} \pm \frac{\sqrt{\left(\frac{1}{RC}\right)^2 - 4 \times \frac{1}{LC}}}{2 \times 1}$$

$$\begin{aligned} S_1, S_2 &= -\frac{1}{2RC} \pm \frac{\sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}}{2} \\ &= -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} \end{aligned}$$

$\omega_0,$ $\boxed{\alpha = \frac{1}{2RC}}$ & $\boxed{\omega_0 = \frac{1}{\sqrt{LC}}}$

When the response is underdamped.

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\sqrt{\alpha^2 - \omega_0^2} = \sqrt{-1} \sqrt{\omega_0^2 - \alpha^2} = j \sqrt{\omega_0^2 - \alpha^2}$$

where $j = \sqrt{-1}$

Now,

$$\boxed{\omega_d = \sqrt{\omega_0^2 - \alpha^2}}$$

ω_d = natural freq.

As we know -

$$\omega_0 = \omega_0 RC$$

$$\therefore RC = \frac{\omega_0}{\omega_0}$$

and

$$\alpha = \frac{1}{2RC} = \frac{\omega_0}{2\omega_0}$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

\therefore exponential damping coefficient -

$$\omega_d = \sqrt{\omega_0^2 - \left(\frac{\omega_0}{2\omega_0}\right)^2}$$

$$\omega_d = \sqrt{\omega_0^2 \left(1 - \frac{1}{\alpha\omega_0}\right)^2}$$

$$\omega_d = \omega_0 \sqrt{1 - \left(\frac{1}{\alpha\omega_0}\right)^2}$$

Natural freq.,

As,

$$s^2 + \frac{1}{RC}s + \frac{1}{LC}$$

We can write this eq^u in terms of α and

ω_0 so eq^u is

$$s^2 + 2\alpha s + \omega_0^2 \quad -(A)$$

or in the form with damping factor

$$s^2 + 2\zeta\omega_0 s + \omega_0^2 \quad -(B)$$

By comparing eqⁿ (A) & (B)

$$\zeta = \frac{d}{\omega_0} = \frac{1}{2Q_0}$$

→ damping factor

Problem-3

(a) The admittance of the parallel RLC ckt.

$$Y = \frac{1}{R} + j \left(\omega C - \frac{1}{\omega L} \right) \quad - \textcircled{1}$$

and $Q_0 = \omega_0 RC = \frac{1}{\sqrt{LC}} RC = R \sqrt{\frac{C}{L}} \times \frac{\sqrt{L}}{\sqrt{C}} = R \frac{\sqrt{LC}}{L}$

$$\boxed{C = \frac{Q_0}{\omega_0 R}} \quad - \textcircled{2}$$

Also


$$Q_0 = \frac{R \sqrt{LC}}{L} = \frac{R}{L \times \omega_0}$$

so, $\boxed{L = \frac{R}{\omega_0 Q_0}} \quad - \textcircled{3}$

from eqⁿ $\textcircled{1}$, $\textcircled{2}$ & $\textcircled{3}$

$$Y = \frac{1}{R} + j \left(\frac{\omega Q_0}{\omega_0 R} - \frac{\omega_0 Q_0}{\omega R} \right)$$
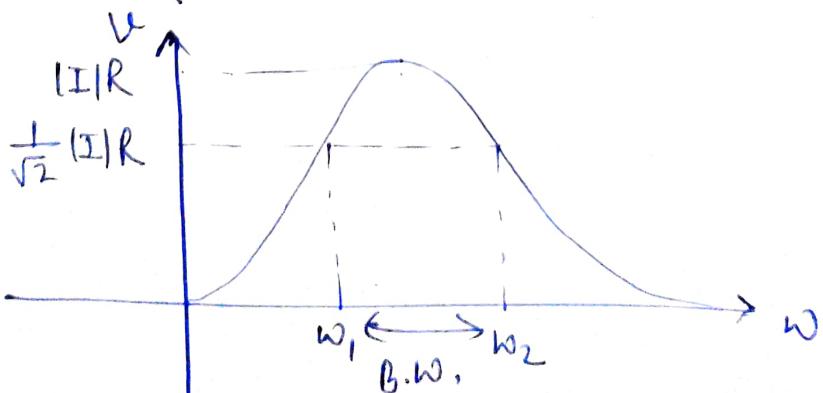
$$Y = \frac{1}{R} + j \frac{Q_0}{R} \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) \quad - \textcircled{4}$$



$$\frac{V}{I} = Z = \frac{1}{Y}, \quad |Y| = \frac{|I|}{|V|} = \frac{|I|}{\frac{1}{\sqrt{2}} |I| R} = \frac{\sqrt{2} |I|}{R} = \frac{\sqrt{2}}{R}$$

V is $\frac{1}{\sqrt{2}}$ times, Y is $\sqrt{2}$ times

for half power freq.

from eqn ④ $|Y| = \frac{\sqrt{2}}{R}$

$$\Rightarrow \left[\frac{1}{R} + \frac{Q_0 j}{R} \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) \right] = \frac{\sqrt{2}}{R}$$

$$\Rightarrow \cancel{\left[1 + Q_0 j \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) \right]} = \frac{\sqrt{2}}{R}$$

$$\Rightarrow Q_0 \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) = \pm 1$$

$$\Rightarrow Q_0 \left(\frac{\omega_1}{\omega_0} - \frac{\omega_0}{\omega_1} \right) = -1$$

and

$$Q_0 \left(\frac{\omega_2}{\omega_0} - \frac{\omega_0}{\omega_2} \right) = +1$$

Solving we have -

$$\omega_1 = \omega_0 \left[\sqrt{1 + \left(\frac{1}{2Q_0} \right)^2} - \frac{1}{2Q_0} \right] \quad (5)$$

$$\omega_2 = \omega_0 \left[\sqrt{1 + \left(\frac{1}{2Q_0} \right)^2} + \frac{1}{2Q_0} \right] \quad (6)$$

$$\begin{aligned} \text{B.W.} &= \omega_2 - \omega_1 \\ &= \omega_0 \left[\sqrt{1 + \left(\frac{1}{2Q_0}\right)^2} + \frac{1}{2Q_0} - \right] \left[\sqrt{1 + \left(\frac{1}{2Q_0}\right)^2} + \frac{1}{2Q_0} \right] \end{aligned}$$

$$\text{B.W.} = \omega_0 \left[\frac{1}{2Q_0} + \frac{1}{2Q_0} \right]$$

$$\text{B.W.} = \omega_0 \left[\frac{1}{Q_0} \right]$$

$$\boxed{\text{B.W.} = \frac{\omega_0}{Q_0}}$$

$$Q_0. \boxed{\text{B.W.} \propto \frac{1}{Q_0}}$$

(b) We have to show

$$\sqrt{\omega_1 \omega_2} = \omega_0 \quad - \quad (7)$$

Square both side.

$$\omega_1 \omega_2 = \omega_0$$

from eqⁿ (5) & (6)

$$\begin{aligned} &\omega_0 \left[\sqrt{1 + \left(\frac{1}{2Q_0}\right)^2} - \frac{1}{2Q_0} \right] \omega_0 \left[\sqrt{1 + \left(\frac{1}{2Q_0}\right)^2} + \frac{1}{2Q_0} \right] \\ &= \omega_0^2 \left[1 + \left(\frac{1}{2Q_0}\right)^2 + \cancel{\frac{1}{2Q_0}} \sqrt{1 + \left(\frac{1}{2Q_0}\right)^2} - \cancel{\frac{1}{2Q_0}} \left[1 + \left(\frac{1}{2Q_0}\right)^2 - \cancel{\frac{1}{2Q_0}} \right] \right] \end{aligned}$$


ω_0

$$\omega_1 \omega_2 = \omega_0^2$$

or

$$\boxed{\omega_0 = \sqrt{\omega_1 \omega_2}}$$

P4

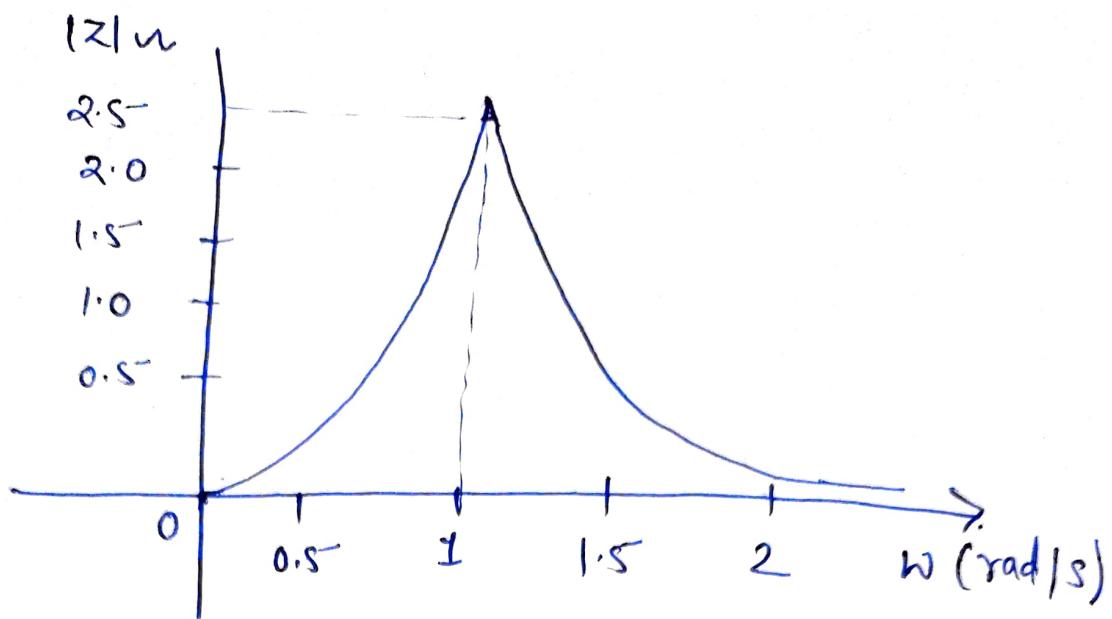

(a)

Resonance frequency $\omega_0 = 1 \text{ rad/s}$. (from graph)

At resonance impedance = Resistance (Ckt fairly resistive)

$$\boxed{R = 2.5 \Omega}$$

(b) AS $\omega_0 = \frac{1}{\sqrt{LC}}$

$$1 = \frac{1}{\sqrt{1 \times C}}$$

$$\sqrt{C} = \frac{1}{1}$$

$$\boxed{C = 1 \text{ F}} \quad \underline{\text{Ans}}$$

$$(c) \quad Q = \omega_0 R C \\ = 1 \times 2.5 \times 1 \\ \boxed{Q = 2.5}$$

~~(b)~~
$$B.W = \frac{\omega_0}{Q_0} = \frac{1}{2.5} = 0.4$$

$$\boxed{B.W = 0.4 \text{ rad/s.}}$$

$$\Rightarrow B.W = \omega_2 - \omega_1 \Rightarrow 0.4 = \omega_2 - \omega_1 \quad -①$$

$$\Delta \quad \omega_0 = \sqrt{\omega_1 \omega_2} \Rightarrow 1 = \sqrt{\omega_1 \omega_2} \Rightarrow 1 = \omega_1 \omega_2$$

$$\omega_2 = \frac{1}{\omega_1} \quad -②$$

from eqⁿ ① & ②

$$0.4 = \frac{1}{\omega_1} - \omega_1$$

$$0.4 = \frac{1 - \omega_1^2}{\omega_1}$$

$$0.4\omega_1 = 1 - \omega_1^2$$

$$\omega_1^2 + 0.4\omega_1 - 1 = 0$$

$$\omega_1 = \frac{-0.4 \pm \sqrt{(0.4)^2 - 4 \times 1 \times (-1)}}{2 \times 1}$$

$$\omega_1 = \frac{-0.4 \pm \sqrt{0.16 + 4}}{2}$$

$$\omega_1 = \frac{-0.4 \pm \sqrt{4.16}}{2}$$

$$\omega_1 = -0.2 \pm 1.01$$


$$\boxed{\omega_1 = 0.81 \text{ rad/s.}}$$

$$\boxed{\omega_2 = \frac{1}{0.81} = 1.23 \text{ rad/s.}}$$

Q F

P-6

The CKT for simple low pass filter.

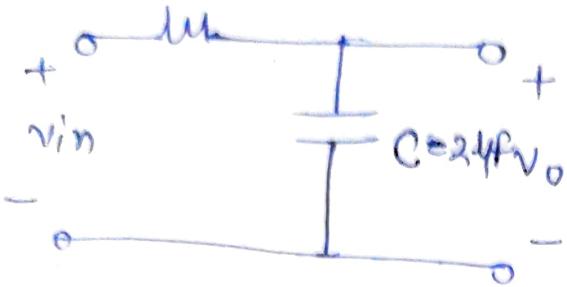

from the circuit

$$v_o(s) = \frac{\frac{1}{sC} \times v_{in}(s)}{\frac{1}{sC} + R} = \frac{\frac{1}{sC}}{\frac{1}{sC} + sR} = \frac{1}{1+sCR} v_{in}(s)$$

$$\frac{v_o(s)}{v_{in}(s)} = \frac{1}{1+sCR}$$

$$\downarrow \\ H(s) = \frac{1}{1+sCR} \Rightarrow H(j\omega) = \frac{1}{1+j\omega CR}$$

~~Amplitude~~ \propto ~~Phase~~

$$|H(j\omega)| = \frac{1}{\sqrt{1+(\omega CR)^2}}$$

At break or cut-off freq.

$$\frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1+(\omega_c R)^2}}$$

$$1+(\omega_c R)^2 = 2$$

$$\omega_c R = 1$$

$$\boxed{\omega_c = \frac{1}{RC}}$$


$$1450 = \frac{1}{R \times C}$$


$$1450 = \frac{1}{2 \times 10^{-6} \times R}$$

$$R = \frac{1}{2 \times 10^{-6} \times 1450}$$

$$R = 0.000344 \times 10^6$$

$$\boxed{R = 344 \Omega}$$

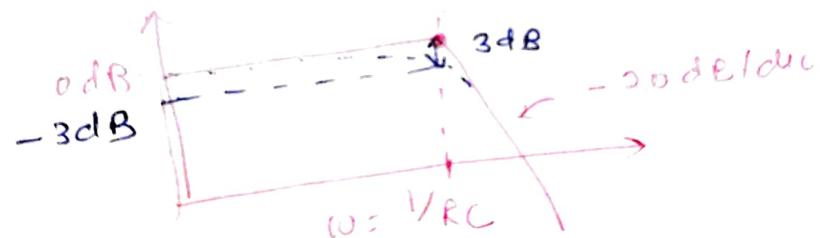


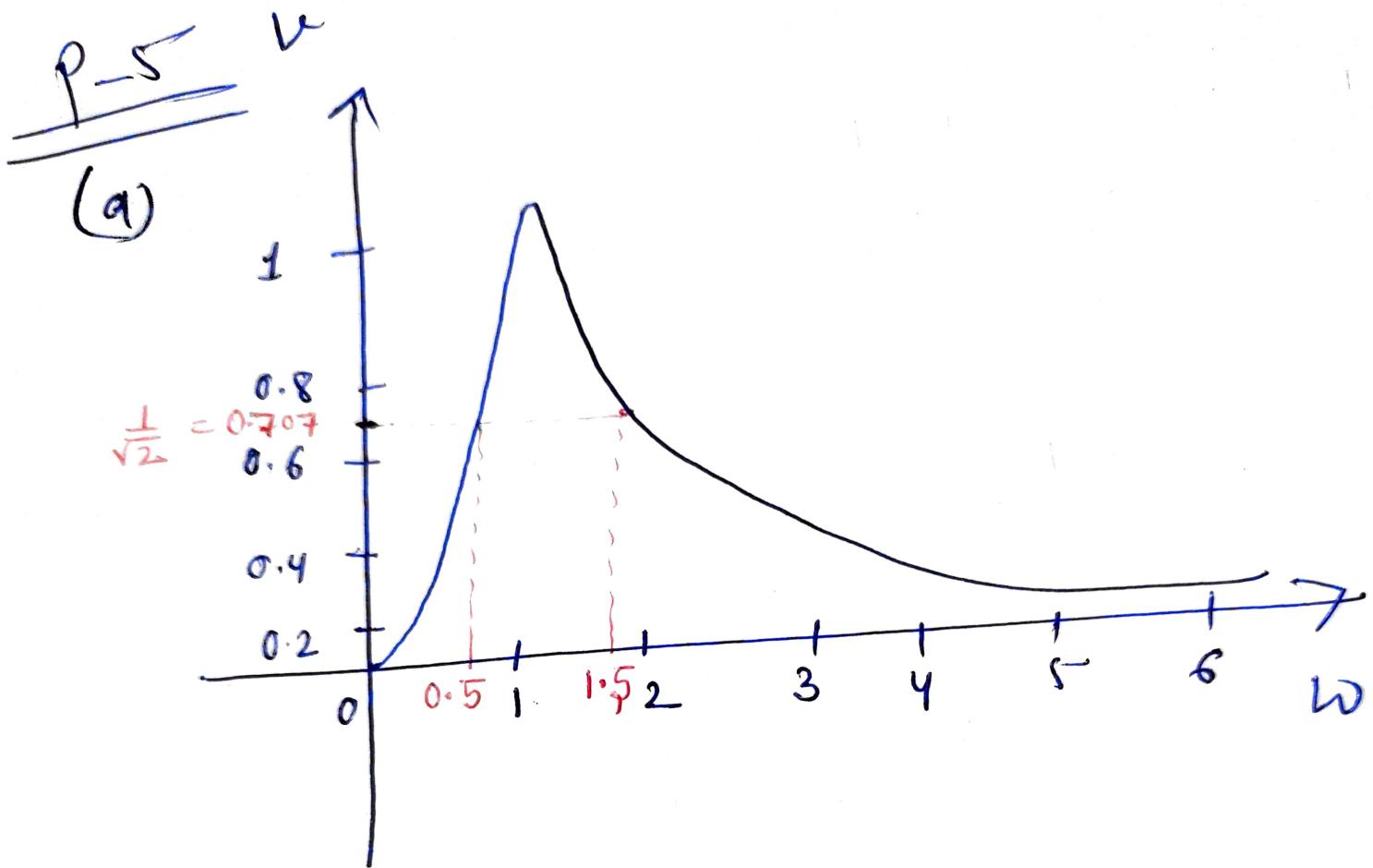

$$BW \approx \omega_2 - \omega_1$$

$$\approx 1.5 - 0.5$$

$$[BW \approx 1 \text{ kHz}]$$

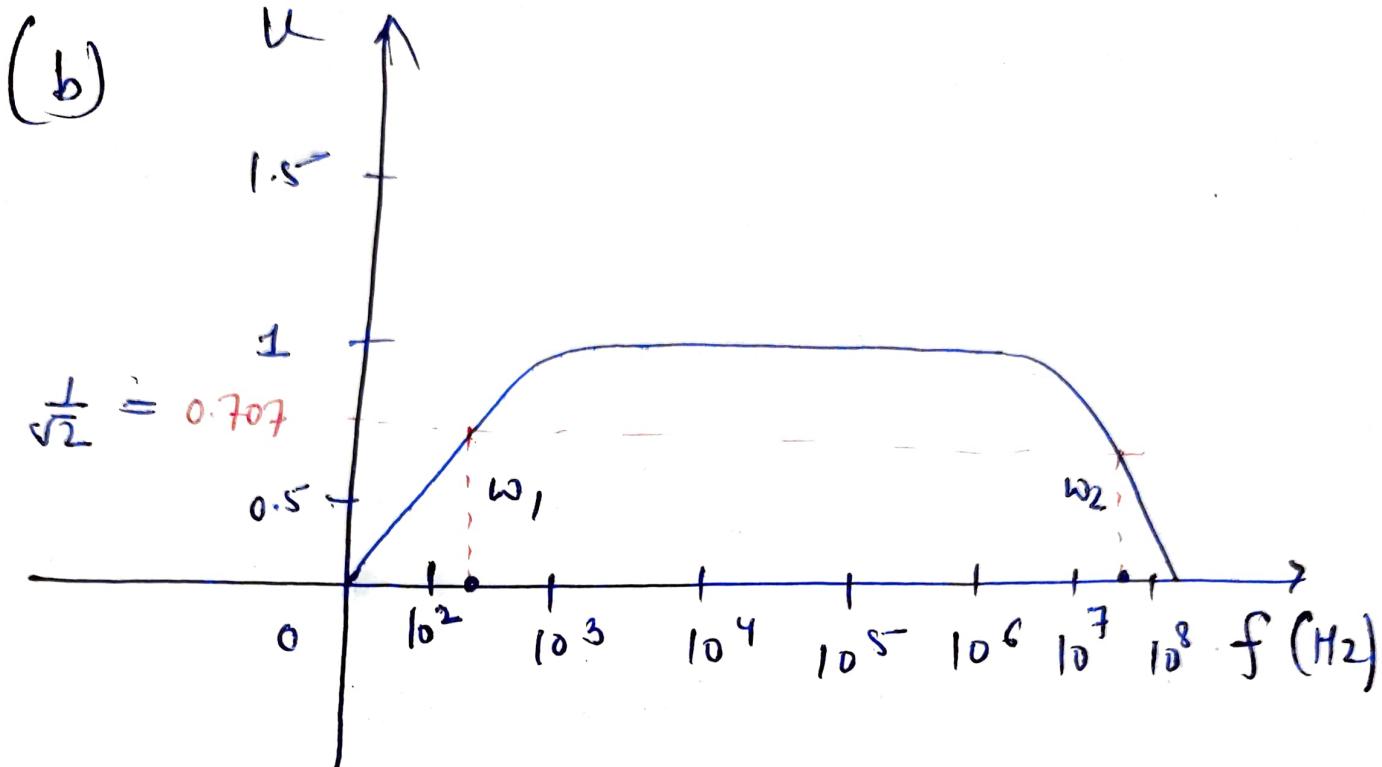

$$\frac{1}{\sqrt{2}} = 0.707$$

$$BW \approx 10^7 - 10^2$$

$$BW \approx 10^7$$

$$BW = 10 \times 10^6$$

$$BW = 10 \text{ MHz}$$