

Tutorial 9

Problem 1)

4. For the circuit in Fig. 15.54, (a) derive an algebraic expression for the transfer function $\mathbf{H}(j\omega) = v_{\text{out}}/i_{\text{in}}$ in terms of circuit components R_1 , R_2 , C_1 , and C_2 ; and (b) evaluate the magnitude of \mathbf{H} at frequencies of 100 Hz, 10 kHz, and 1 MHz for case where $R_1 = 20 \text{ k}\Omega$, $R_2 = 5 \text{ k}\Omega$, $C_1 = 10 \text{ nF}$, and $C_2 = 40 \text{ nF}$.

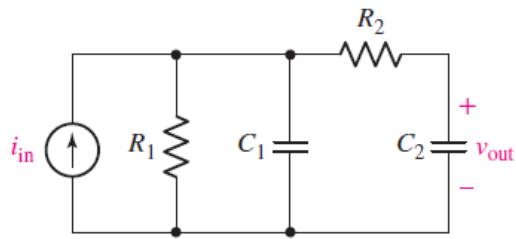


FIGURE 15.54

Problem 2)

6. For the circuit in Fig. 15.56, (a) determine the transfer function $\mathbf{H}(j\omega) = V_{\text{out}}/V_{\text{in}}$ in terms of circuit parameters R_1 , R_2 , and C ; (b) determine the magnitude and phase of the transfer function at $\omega = 0$, $3 \times 10^4 \text{ rad/s}$, and as $\omega \rightarrow \infty$ for the case where circuit values are $R_1 = 500 \Omega$, $R_2 = 40 \text{ k}\Omega$, and $C = 10 \text{ nF}$.

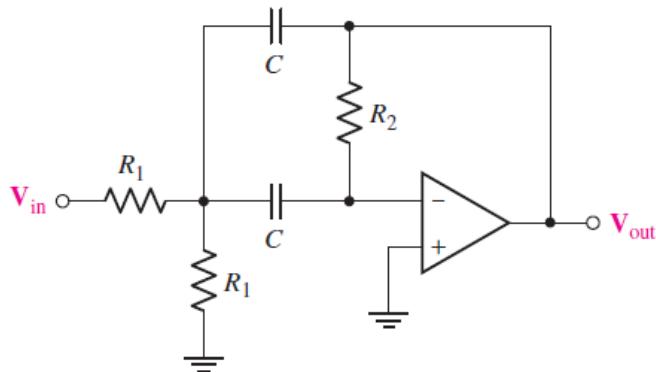


FIGURE 15.56

Problem 3)

8. Sketch the Bode magnitude and phase plots for the following functions:
 (a) $3 + 4s$; (b) $\frac{1}{3 + 4s}$.

Problem 4)

9. For the following functions, sketch the Bode magnitude and phase plots:

$$(a) 25\left(1 + \frac{s}{3}\right)(5 + s); (b) \frac{0.1}{(1 + 5s)(2 + s)}.$$

Problem 5)

10. Use the Bode approach to sketch the magnitude of each of the following response

$$\frac{4}{s^3 + 7s^2 + 12s}.$$

Problem 6)

11. If a particular network is described by transfer function $H(s)$, plot the magnitude and phase Bode plot

$$(a) \frac{s + 300}{s(5s + 8)}$$


$$H(s) = 3 + 4s = 3(1 + s/3\pi) = 3(1 + \frac{s}{0.75})$$

$$20\log(3) = +9.5 \text{ dB}$$

Q8(a)

Semi-log Paper for Bode Plots

linear scale
dB

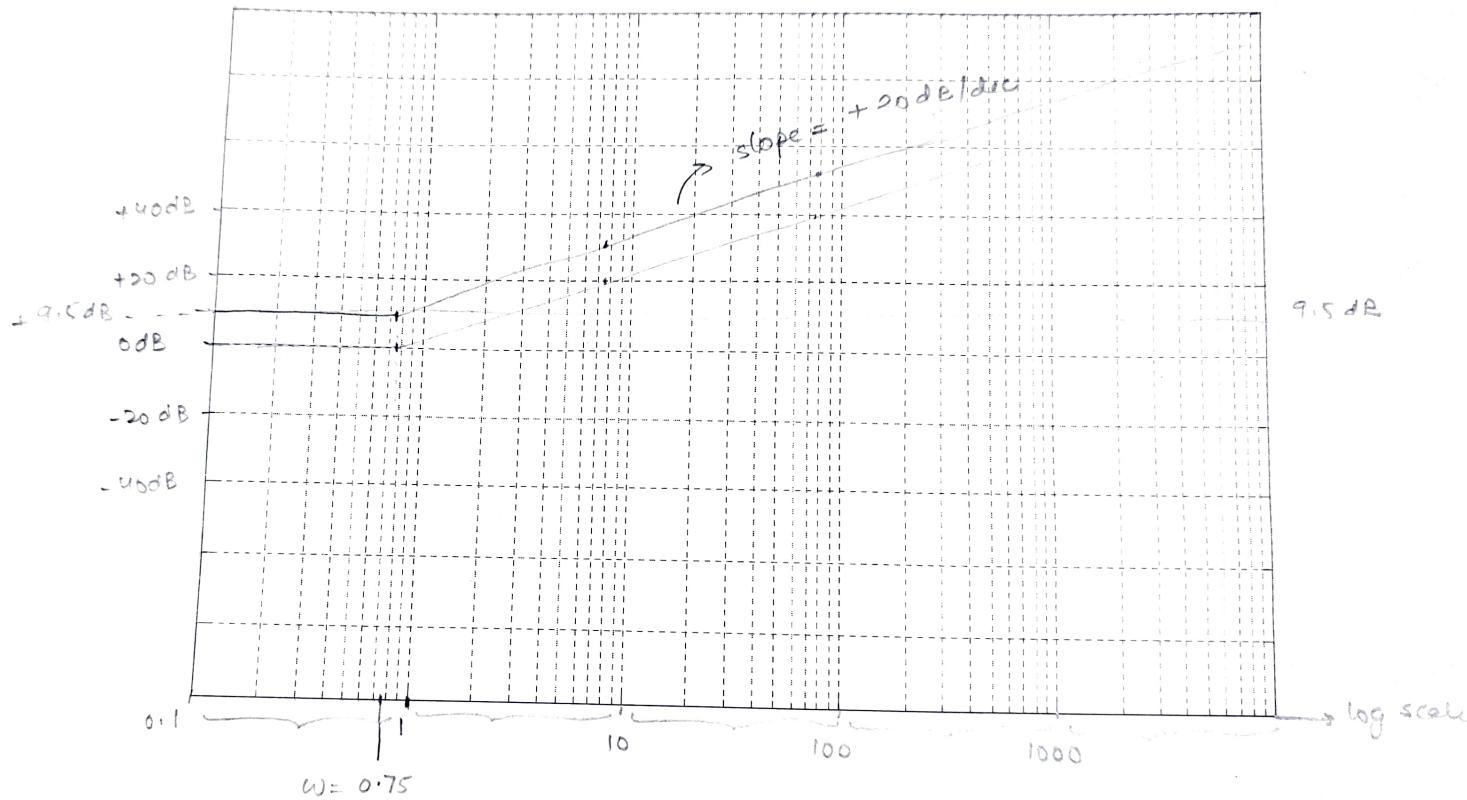


P-3 (Q-8) (q)

$$H(s) = \frac{3}{s} \left(1 + \frac{4}{3}s \right) + \frac{3}{s} \left(1 + \frac{s}{\left(\frac{3}{4}\right)} \right)$$

$LH(j\omega)$

Semi-log Paper for Bode Plots

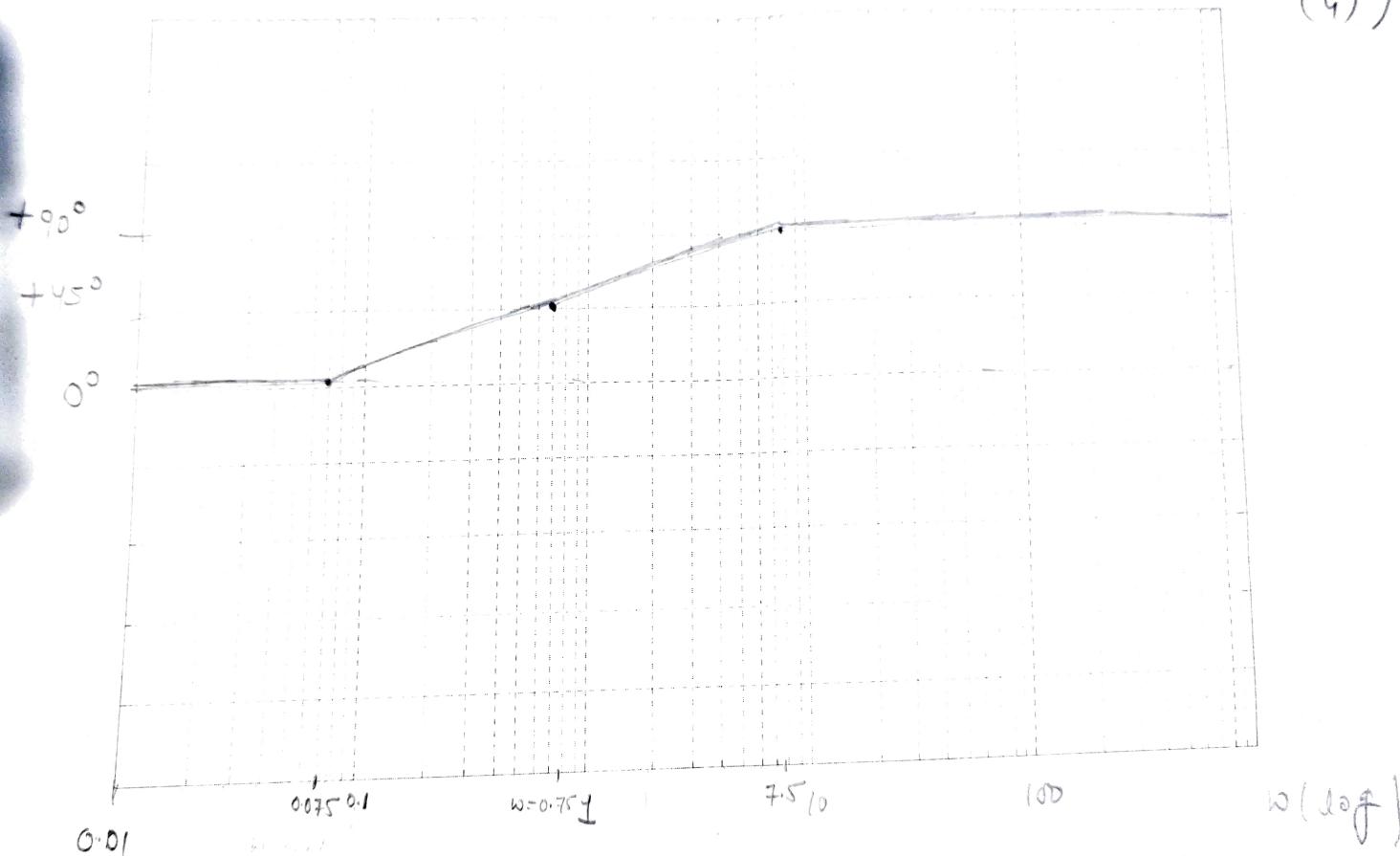


Q9(a)

$L(j\omega)$

Semi-log Paper for Bode Plots


$$125 \left(1 + \frac{s}{3}\right) \left(1 + \frac{s}{5}\right)$$

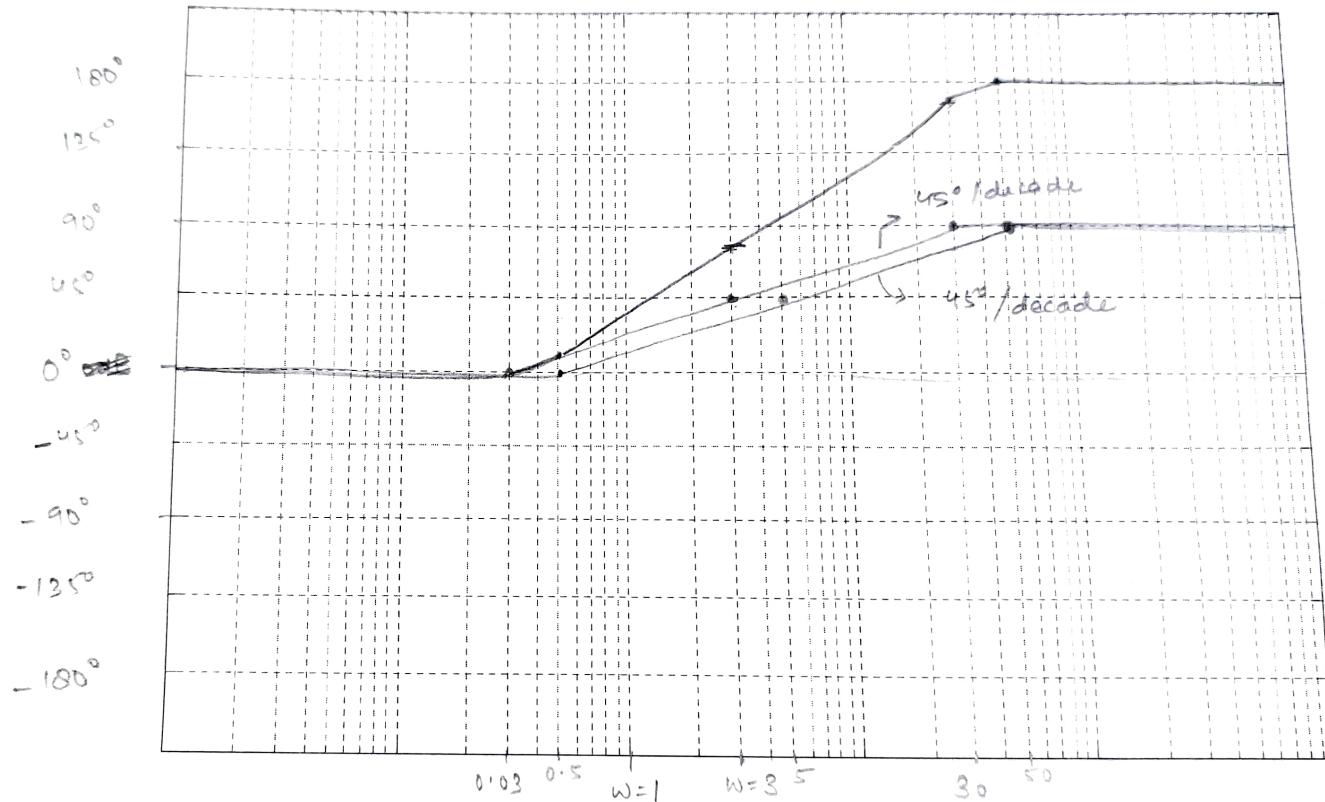A block diagram showing a feedback control system. The forward path has a gain of 125. The feedback path consists of two parallel branches, each with a pole at $s = -3$ and $s = -5$.



Q9(a)

Semi-log Paper for Bode Plots

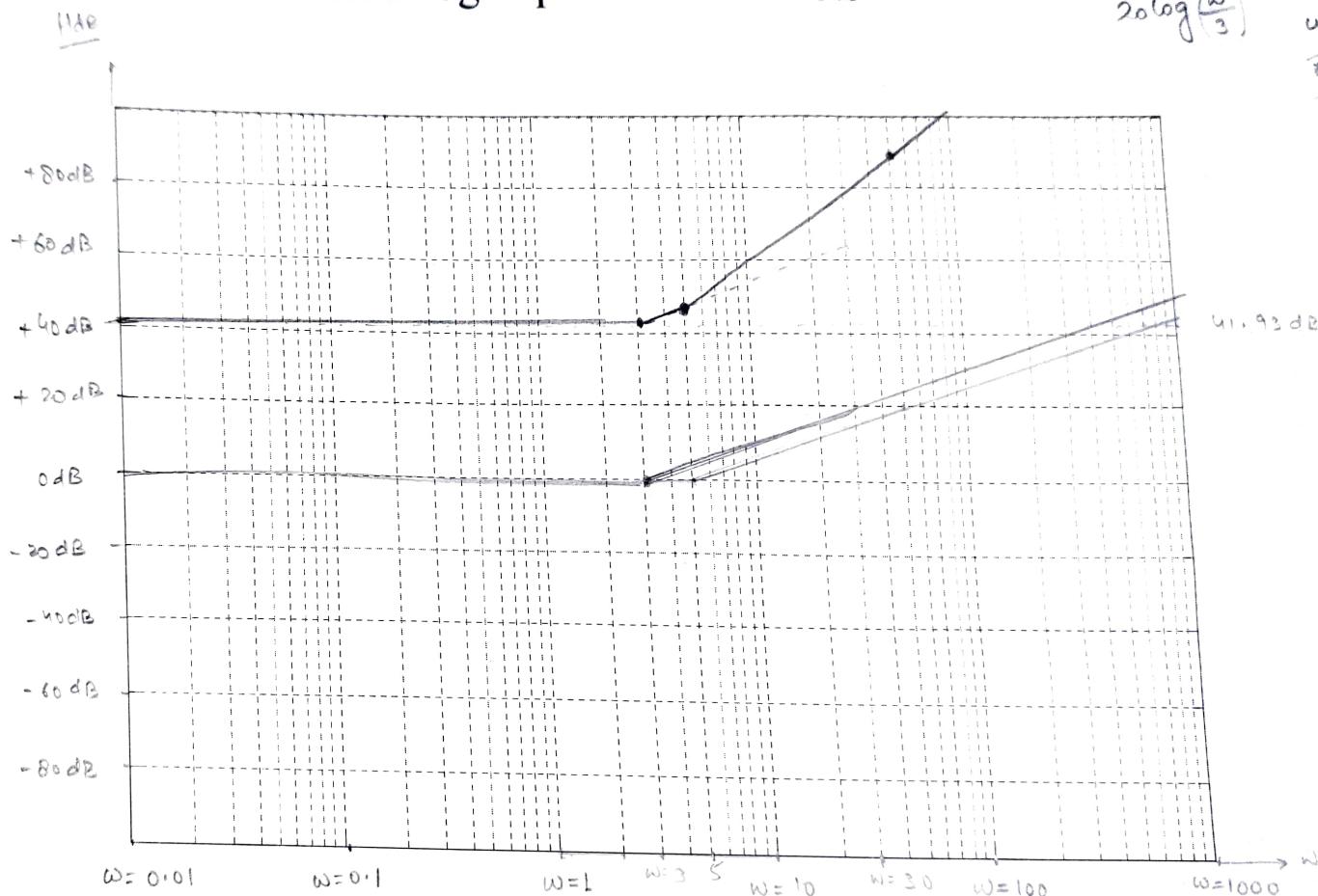

Q11

Semi-log Paper for Bode Plots

$$\frac{37.5(1 + \frac{s}{300})}{s(1 + \frac{s}{8/15})}$$


$$\textcircled{1} 20\log(37.5) = 31.5 \text{ dB}$$

$$\textcircled{2} \left(\frac{1}{s}\right)^n \Rightarrow -20n\log(\omega)$$

$$\textcircled{3} \omega = 1 \text{ rad/s}$$

$$\textcircled{4} \frac{1}{1 + \frac{s}{8/15}}$$

$$(1 + \frac{s}{300})$$

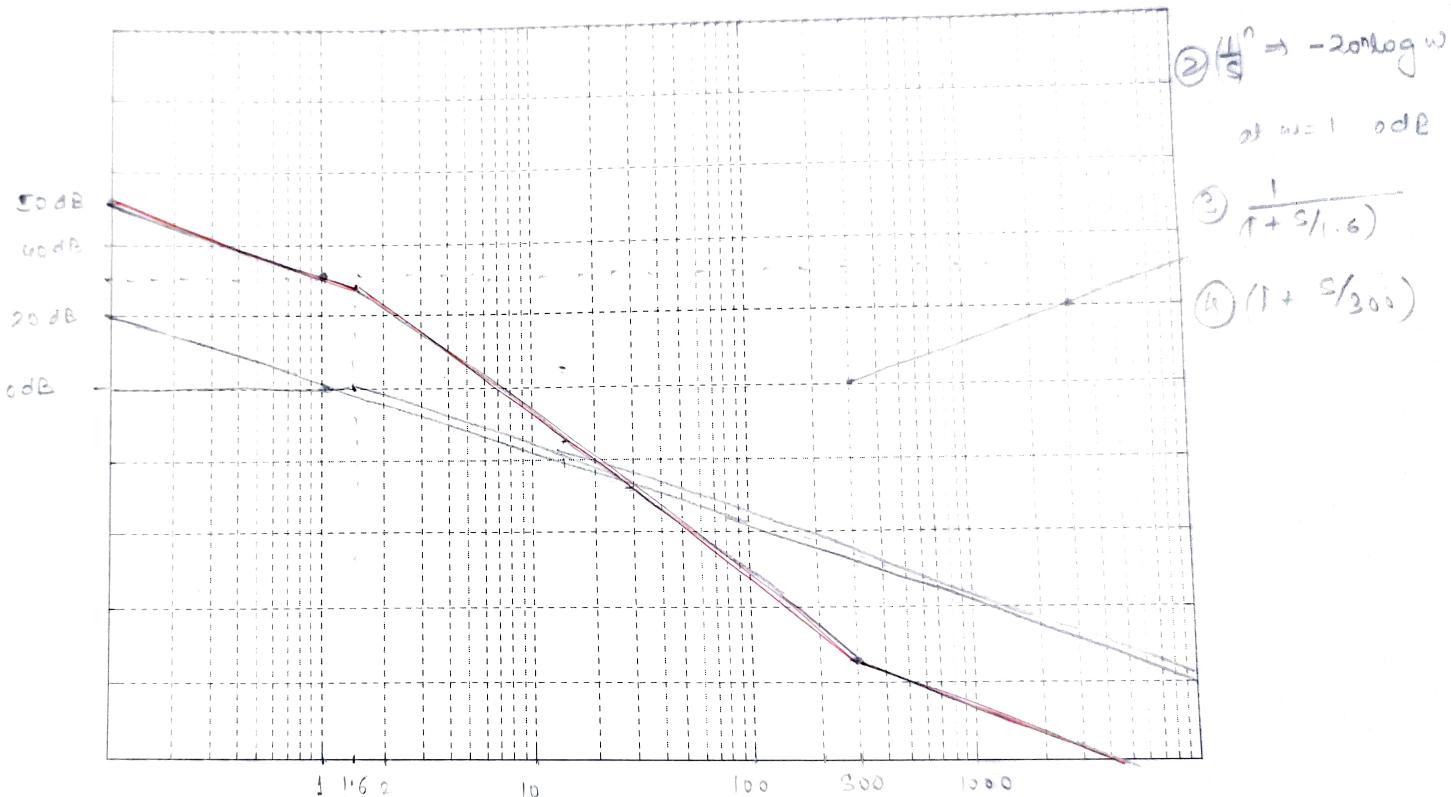


Q11

 $\angle H(j\omega)$

Semi-log Paper for Bode Plots
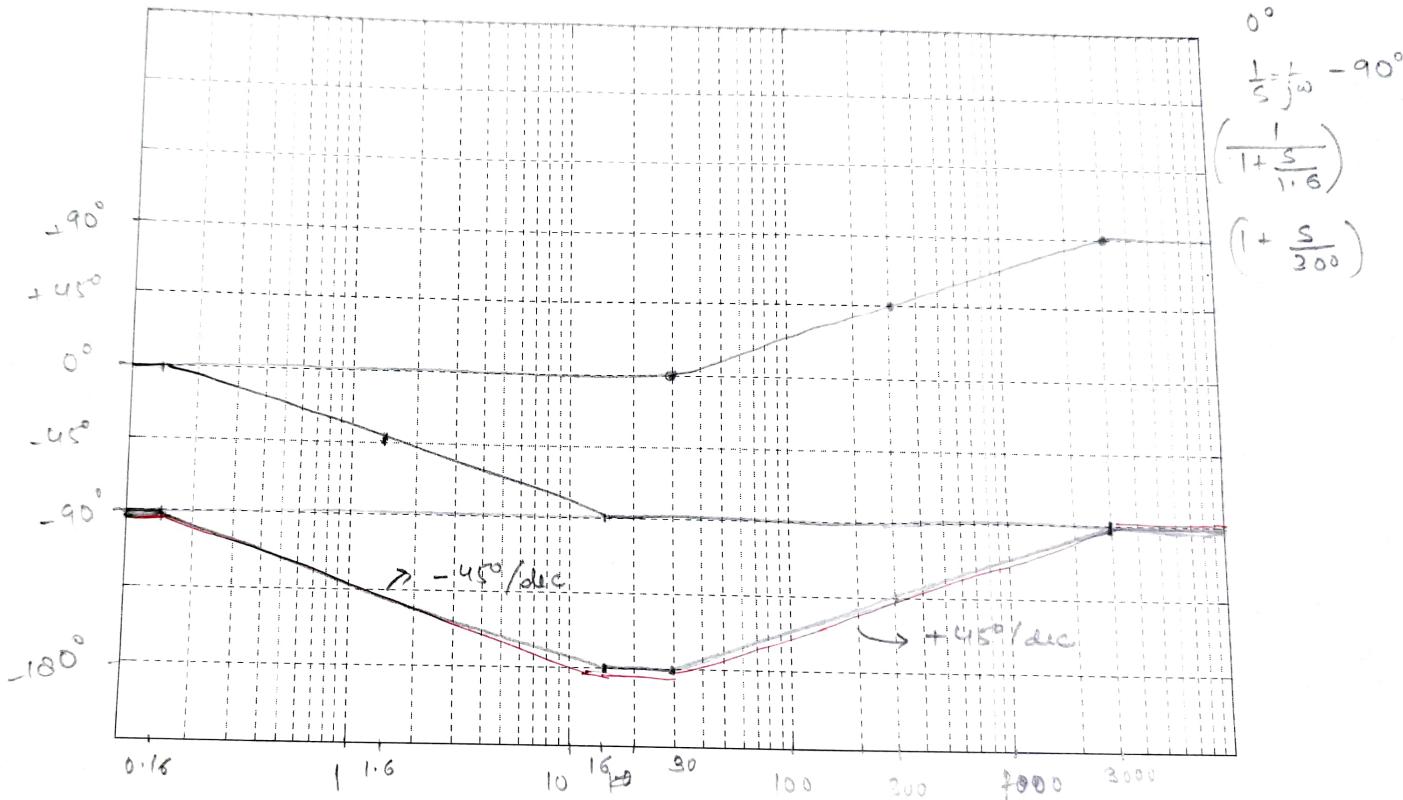
$$\frac{37.5(1 + \frac{s}{200})}{s(1 + \frac{s}{1.6})}$$




Q9(b)

$\angle H(j\omega)$

$$\frac{0.05}{(1 + s/0.1)(1 + s/2)}$$

Semi-log Paper for Bode Plots

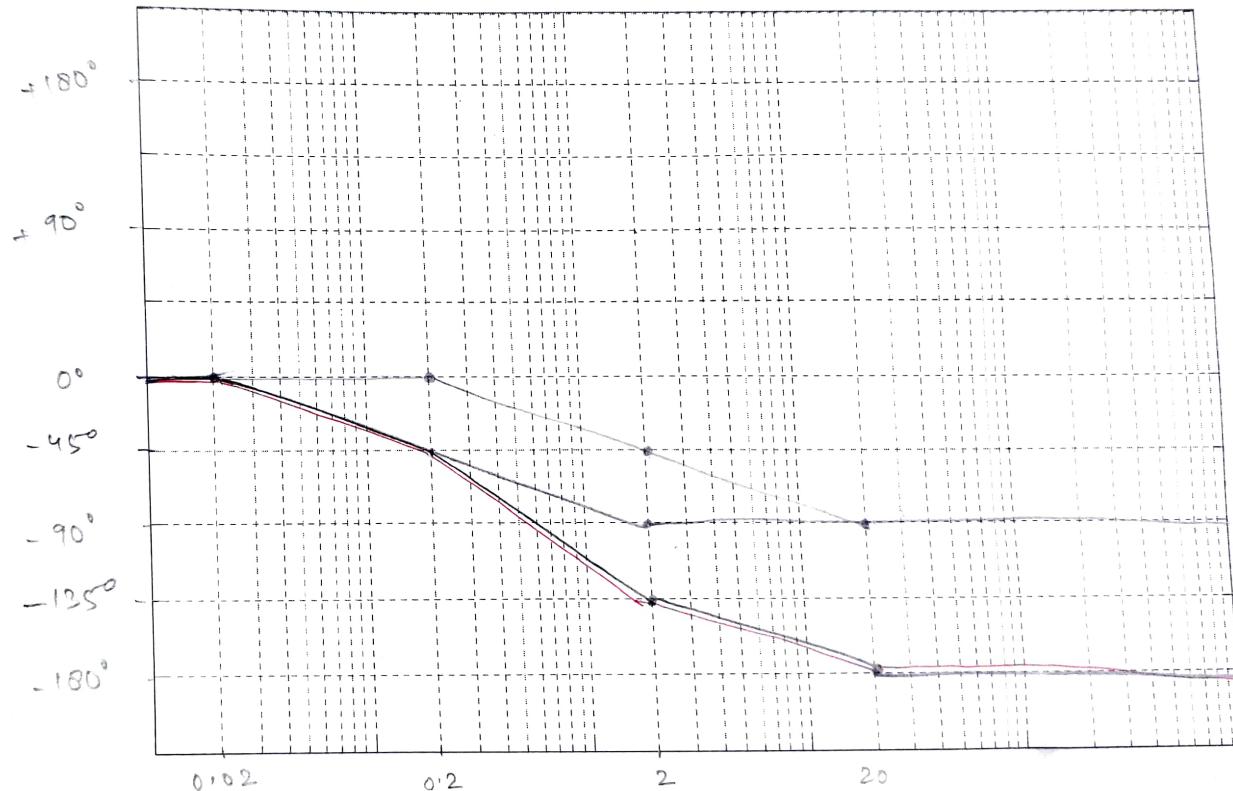


Q9(b)

$$\frac{0.05}{(1 + s/0.2)(1 + s/2)}$$

Semi-log Paper for Bode Plots

H_{dB}

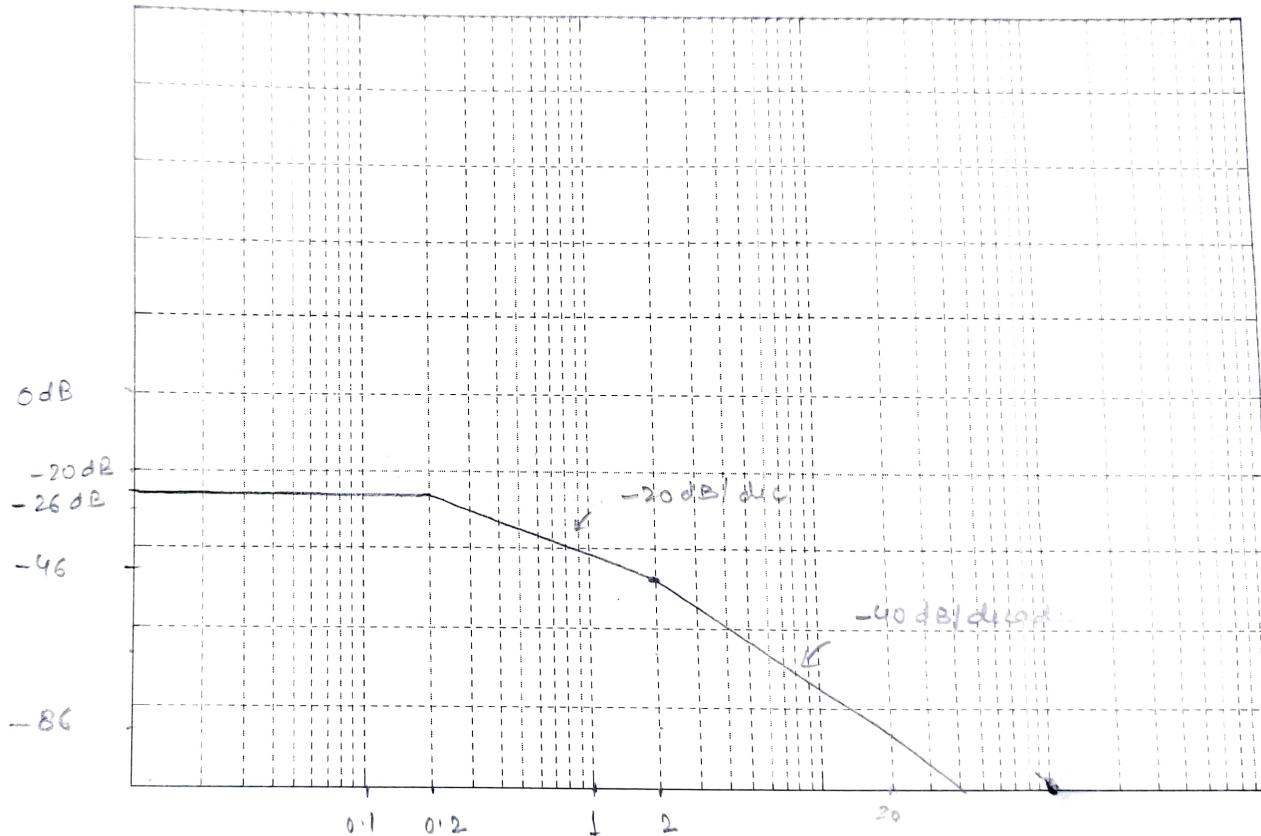

Q-10 (P-5)

$$H(s) = \frac{4}{s^3 + 7s^2 + 12s}$$

$$= \frac{4}{s(s^2 + 7s + 12)} = \frac{4}{s(s+3)(s+4)}$$

$$= \frac{4}{12s \left(1 + \frac{s}{3}\right) \left(1 + \frac{s}{4}\right)} = \frac{1}{3s \left(1 + \frac{s}{3}\right) \left(1 + \frac{s}{4}\right)}$$


$$H(s) = \frac{0.33}{s \left(1 + \frac{s}{3}\right) \left(1 + \frac{s}{4}\right)}$$

$$0.33 : 20 \log(0.33) = -9.62 \text{ dB}$$

$$\left(1 + \frac{s}{3}\right) : \text{corner freq. } w_c = 3 = -20 \text{ dB}$$

$$\left(1 + \frac{s}{4}\right) : \text{corner freq. } w_c = 4 = -20 \text{ dB.}$$

$|H(j\omega)| \text{dB}$

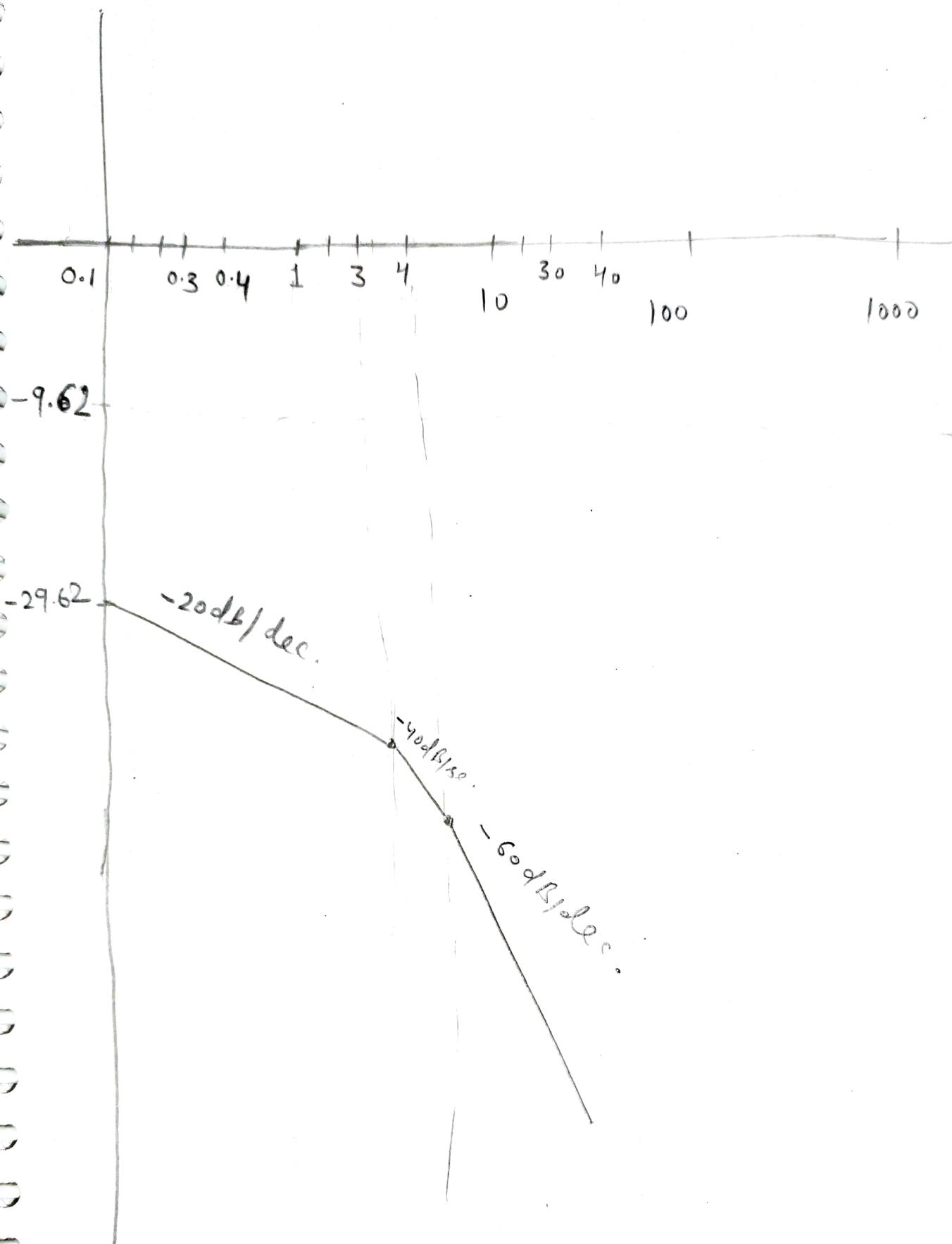

$\angle H(j\omega)$  0° 0.1 0.3 0.4 1 3 4 10 30 40 100 $\omega(\log)$ -45° -90° -166.67 -180° -182.93 -270 τ_1

Q-8 (b)


$$H(s) = \frac{1}{3+4s}$$



$$\begin{aligned} H(s) &= \frac{1}{3} \left(\frac{1}{1 + \frac{4s}{3}} \right) \\ &= \frac{1}{3} \left(\frac{1}{1 + \frac{s}{\frac{3}{4}}} \right) \end{aligned}$$


$\therefore 20 \log (k) = -9.54 \text{ dB}$

$$\left(1 + \frac{s}{\left(\frac{3}{4}\right)}\right)$$

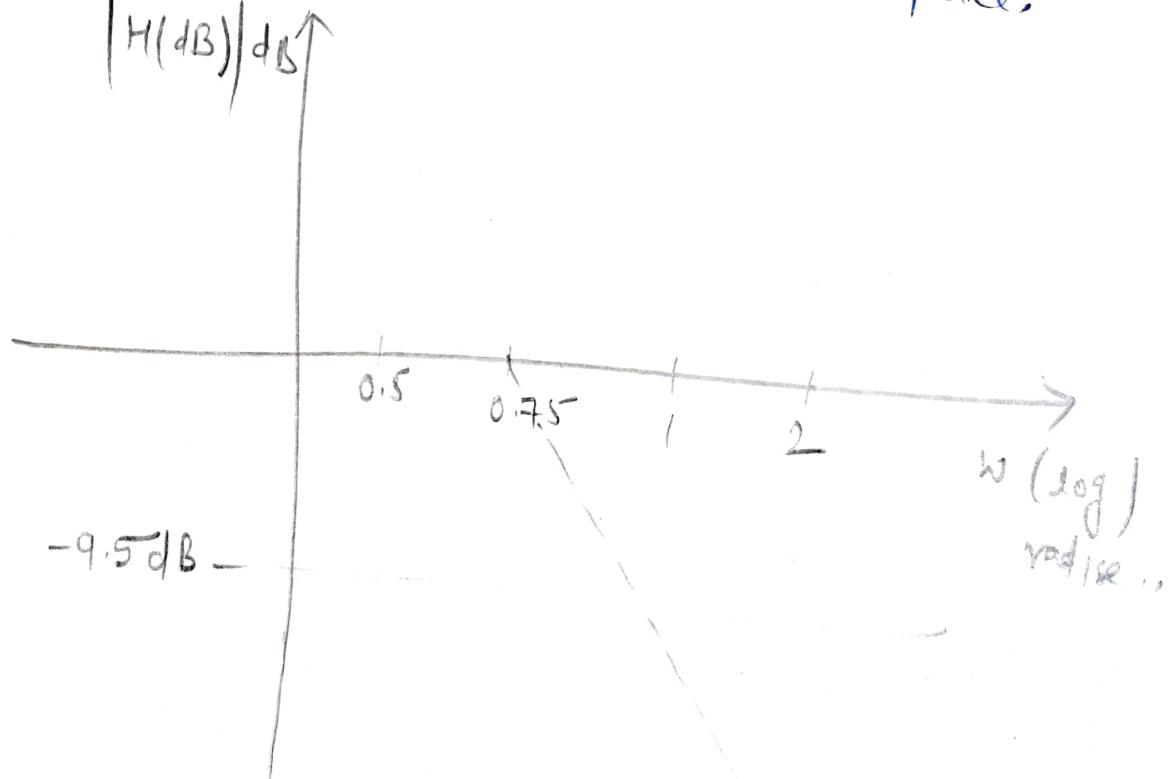: corner freq. $\omega_c = 0.75^\circ = -20 \text{ dB/dec.}$



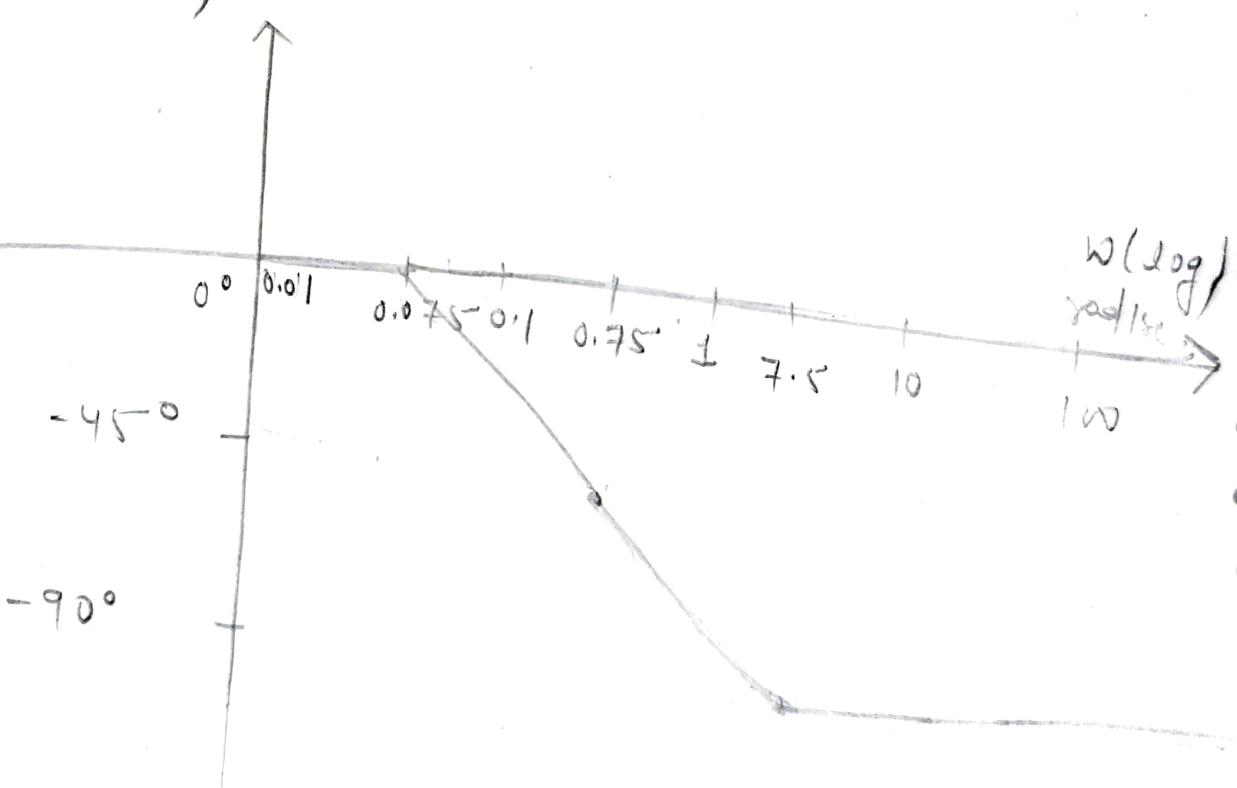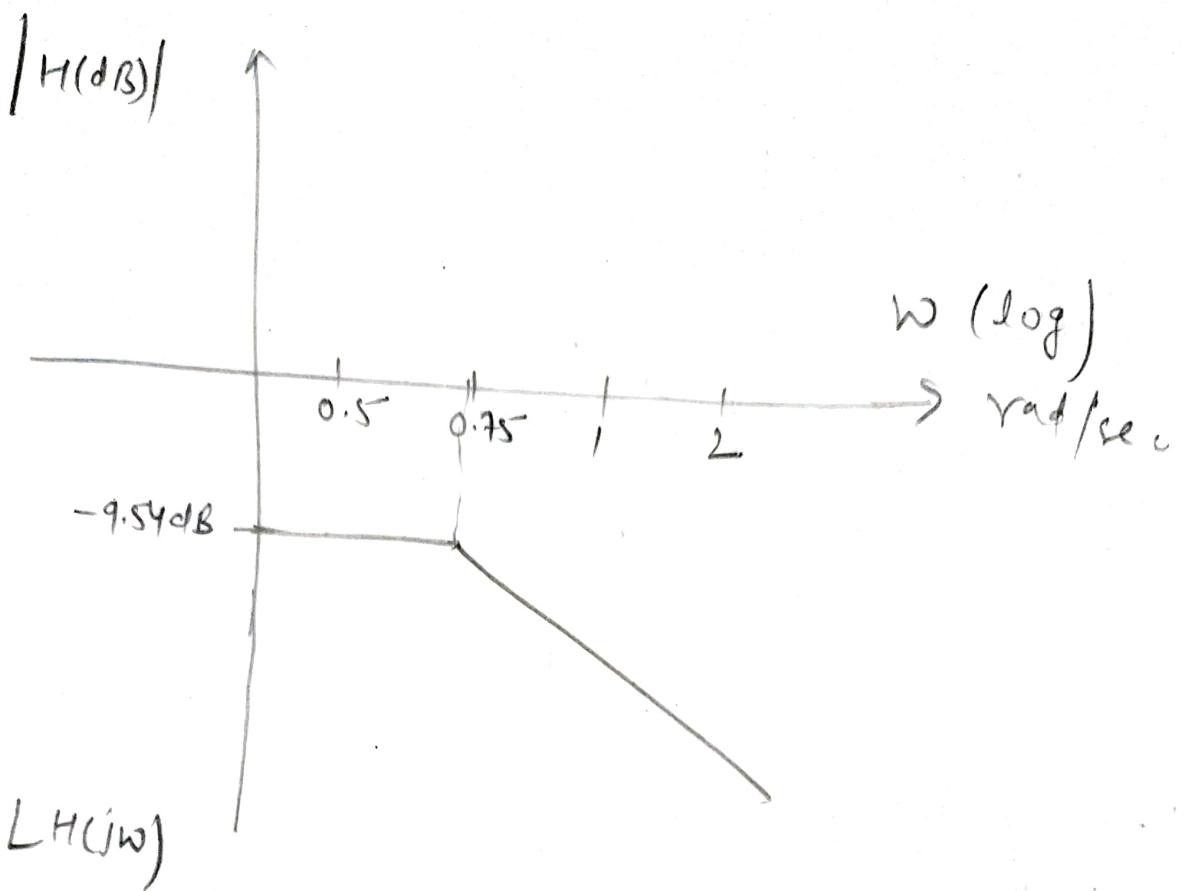

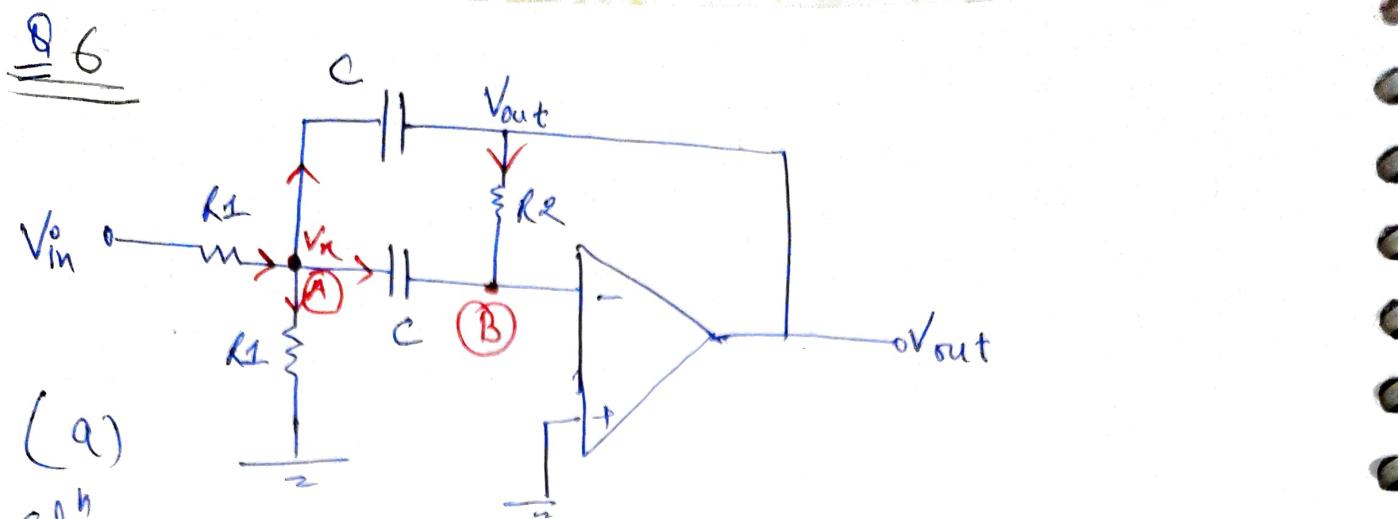

(a)

Solⁿ

KCL at node A

$$\frac{V_{in} - V_x}{R_1} = (V_x - V_{out}) SC + \frac{V_x}{R_1} + V_x SC$$

$$\frac{V_{in}}{R_1} + V_{out} SC = 2V_x SC + \frac{V_x}{R_1} + \frac{V_x}{R_1}$$

$$\frac{V_{in} + V_{out} SC R_1}{R_1} = \frac{(2SC R_1 + 2)}{R_1} V_x$$

$$V_x = \frac{V_{in} + V_{out} SC R_1}{2 + 2SC R_1}$$

KCL at node B

$$(V_x - 0) SC + \frac{V_{out} - 0}{R_2} = 0$$

$$\frac{V_{in} \times SC + V_{out} S^2 C^2 R_1}{2(1+SC R_1)} + \frac{V_{out}}{R_2} = 0$$

$$\frac{V_{out}}{R_2} = -\frac{V_{in} s C}{2(1+sCR_1)} - \frac{V_{out} s^2 C^2 R_1}{2(1+sCR_1)}$$

$$V_{out} = -\frac{V_{in} s C R_2}{2(1+sCR_1)} - \frac{V_{out} s^2 C^2 R_1 R_2}{2(1+sCR_1)}$$

$$V_{out} \left[1 + \frac{s^2 C^2 R_1 R_2}{2(1+sCR_1)} \right] = -\frac{V_{in} s C R_2}{2(1+sCR_1)}$$

$$V_{out} \left[2(1+sCR_1) + s^2 C^2 R_1 R_2 \right] = -V_{in} s C R_2$$

$$H(s) = \boxed{\frac{V_{out}}{V_{in}}} = \frac{-sC R_2}{2(1+sCR_1) + s^2 C^2 R_1 R_2}$$

$$H(j\omega) = \frac{-j\omega C R_2}{2(1+j\omega C R_1) + (-\omega^2 C^2 R_1 R_2)}$$

$$H(j\omega) = \frac{-j\omega C R_2}{2(1+j\omega C R_1) - \omega^2 C^2 R_1 R_2}$$

$$|H(j\omega)| = \frac{\omega C R_2}{\sqrt{(2-\omega^2 C^2 R_1 R_2)^2 + (2\omega C R_1)^2}}$$

At $\omega=0$

$$\boxed{|H(j\omega)| = \frac{0}{\sqrt{(2-0)^2 + (0)^2}} = 0}$$

$$|LH(j\omega)| = \sqrt{0 - \tan^2 \left(\frac{2\omega CR}{2 - \omega^2 C^2 R^2 L} \right)}$$

at $\omega = 0$

$$\boxed{|LH(j\omega)| = 0^\circ} \quad | \text{Phase can not be determined}|$$

$$|H(j\omega)| = \frac{3 \times 10^4 \times 10 \times 10^{-9} \times 40 \times 10^3}{\sqrt{(2 - (3 \times 10^4))^2 \times (10 \times 10^{-9})^2 \times 40 \times 10^3 \times 500} + (2 \times 3 \times 10^4 \times 10 \times 10^{-9} \times 500)^2}$$

$$= \frac{12}{\sqrt{(2 - 0.18)^2 + (0.3)^2}}$$

$$|H(j\omega)| = 6.507$$

$$LH(j\omega) = -\tan^{-1} \left(\frac{2 \times 3 \times 10^4 \times 10^{-8} \times 500}{(2 - 0.18)^2} \right)$$

$$= -\tan^{-1} \left(\frac{3000 \times 10^{-4}}{3.3} \right)$$

$$= -\tan^{-1} \left(\frac{0.3}{3.3} \right)$$

$$\boxed{|H(j\omega)| = -5.199^\circ} \quad \omega = 3 \times 10^4 \text{ rad/s.}$$

$$|H(j\omega)| \Big|_{\omega=\alpha} = \frac{\omega C R_2}{\sqrt{\left(\frac{Q}{\omega^2} - C^2 R_1 R_2\right)^2 + \left(\frac{2CR_1}{\omega^2}\right)^2}}$$

$$\boxed{|H(j\omega)| = \frac{1}{\alpha} = 0}$$

$|H(j\omega)|$ = not defined

TUTORIAL - 9


Given,

$$R_1 = 20 \text{ k}\Omega$$

$$R_2 = 5 \text{ k}\Omega$$


$$C_1 = 10 \text{ nF}$$

$$C_2 = 40 \text{ nF}$$

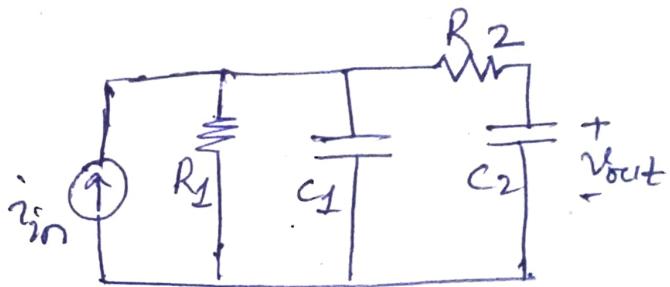

$$Z_L = R_2 \parallel \frac{1}{j\omega C_1}$$
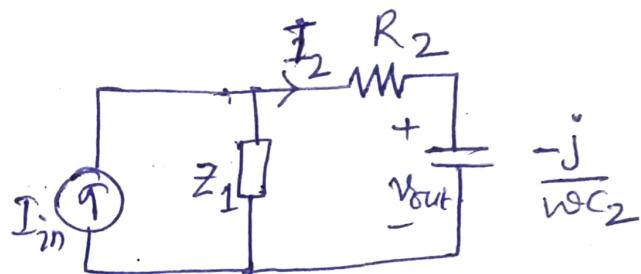
$$\therefore Z_L = \frac{R_1}{1 + j\omega R_1 C_1}$$



By using current division rule

$$I_2 = \frac{Z_1}{Z_1 + R_2 + \frac{1}{j\omega C_2}} \times I_{in}$$

$$\Rightarrow I_2 = \frac{Z_1 j\omega C_2}{j\omega C_2 Z_1 + j\omega C_2 R_2 + 1} I_{in}$$

By using ohm's law,

$$V_{out} = \frac{1}{j\omega C_2} I_2$$

$$\therefore V_{out} = \frac{1}{j\omega C_2} \times \frac{Z_1 j\omega C_2}{j\omega C_2 Z_1 + j\omega C_2 R_2 + 1} I_{in}$$

$$\Rightarrow \frac{V_{out}}{I_{in}} = \frac{\left(R_1 / 1 + j\omega R_1 C_1 \right)}{j\omega C_2 \left(\frac{R_1}{1 + j\omega R_1 C_1} + R_2 \right) + 1}$$

$$\Rightarrow \frac{V_{out}}{I_{in}} = \frac{R_1}{j\omega C_2(R_1 + R_2 + jR_1 R_2 \omega C_1) + 1 + j\omega R_1 C_1}$$

$$\Rightarrow \frac{V_{out}}{I_{in}} = \frac{R_1}{j\omega C_2 R_1 + j\omega C_2 R_2 - R_1 R_2 C_1 C_2 \omega^2 + j\omega R_1 C_1 + 1}$$

$$\Rightarrow \frac{V_{out}}{I_{in}} = \frac{R_1}{(1 - R_1 R_2 C_1 C_2 \omega^2) + j(\omega C_1 R_1 + \omega C_2 R_2 + \omega R_1 C_1)}$$

$$\Rightarrow H(j\omega) = \frac{R_1}{(1 - \omega^2 R_1 R_2 C_1 C_2) + j(R_1 C_1 + R_2 C_2 + R_1 C_1)\omega}$$

$$\Rightarrow H(j\omega) = \frac{20K}{(1 - \omega^2 \times 4 \times 10^{-8}) + j\omega (1.2 \times 10^{-3})}$$

(b) If $f = 100\text{Hz}$

$$\omega = 2\pi f \Rightarrow \omega = 628.318 \text{ rad/sec}$$

$$\therefore H(j\omega) = \frac{20K}{0.989 + j0.754} = 16131.36 \angle -37.45^\circ$$

$$\boxed{\left| H(j\omega) \right|_{f=100\text{Hz}} = 16131.3623}$$

$$\text{If } f = 10\text{KHz} \Rightarrow \omega = 62831.853 \text{ rad/sec}$$

$$\therefore H(j\omega) = \frac{20K}{-156.914 + j75.398}$$

If $f = 1 \text{ MHz} \Rightarrow \omega = 6283185.307 \text{ rad/sec}$

$$\therefore H(j\omega) = \frac{20k}{-1579135.704 + j2539.822}$$

$$H(j\omega) = 0.01266 \angle -179.726^\circ$$

$$\therefore \boxed{\left| H(j\omega) \right|_{f=1\text{MHz}} = 0.01266}$$

2) Given, $H(s) = 3 + 4s$

$$= 3 \left[1 + \frac{s}{\frac{3}{4}} \right]$$

gain, $K = 3$ & cutt.-off frequency $\omega_c = \frac{3}{4} \text{ rad/sec}$

→ One zero at $s = -\frac{3}{4}$

→ no pole or zero is present at the origin.
So the starting slope will be 0 dB/dec.

starting point, $20\log(3) \pm 20 \times 0 = 9.54 \text{ dB}$

$$H(\omega) = 3 + 4j\omega$$

$$|H(\omega)| = \sqrt{(3^2) + (4\omega)^2}$$

$$|H(j\omega)|_{\text{dB}} = 20\log(|H(\omega)|)$$